 


INTRODUCTION TO REVERSIBLE LOGIC SYNTHESIS



Robert Wille

Johannes Kepler University Linz, Austria

robert.wille@jku.at

FURTHER READING

- **Good overview (state-of-the-art report of the COST Action):**

<https://github.com/COST-IC1405/wg3-soar-report/blob/master/README.md>

- **Embedding**

Embedding of Large Boolean Functions for Reversible Logic, JETC 2016

Make It Reversible: Efficient Embedding of Non-reversible Functions. DATE 2017

- **Transformation-based Synthesis**

A Transformation Based Algorithm for Reversible Logic Synthesis, DAC 2003

A fast symbolic transformation based algorithm for reversible logic synthesis, RC 2016.

- **BDD-based Synthesis**

BDD-based Synthesis of Reversible Logic for Large Functions, DAC 2009

- **One-pass Synthesis**

One-pass Design for Reversible Circuits: Combining Embedding and Synthesis for Reversible Logic, TCAD 2017

- **QMDD Data-structure**

QMDDs: Efficient Quantum Function Representation and Manipulation, TCAD 2016

Implementation available at <http://www.informatik.uni-bremen.de/agra/eng/qmdd.php>

- **SyReC HDL**

SyReC: A Hardware Description Language for the Specification and Synthesis of Reversible Circuits, INTEGRATION 2016

OUTLINE

- What is Reversible Logic?

- ~~■ Why Reversible Logic?~~ → Tomorrow (Applications)


- How to Design of Reversible Logic?

- What's Next?


ALTERNATIVE: REVERSIBLE LOGIC

- Computations are reversible (bijective)
 - Same number of inputs/outputs
 - 1:1 mapping

AND-Gate
(irreversible)

 


Reversible
Logic

 

REVERSIBLE CIRCUITS

 - Fanout and feedback not directly allowed
- Cascade of reversible gates



OUTLINE


- What is Reversible Logic?

- ~~■ Why Reversible Logic?~~ → Tomorrow (Applications)

- How to Design of Reversible Logic?

- What's Next?

HOW TO DESIGN REVERSIBLE LOGIC?

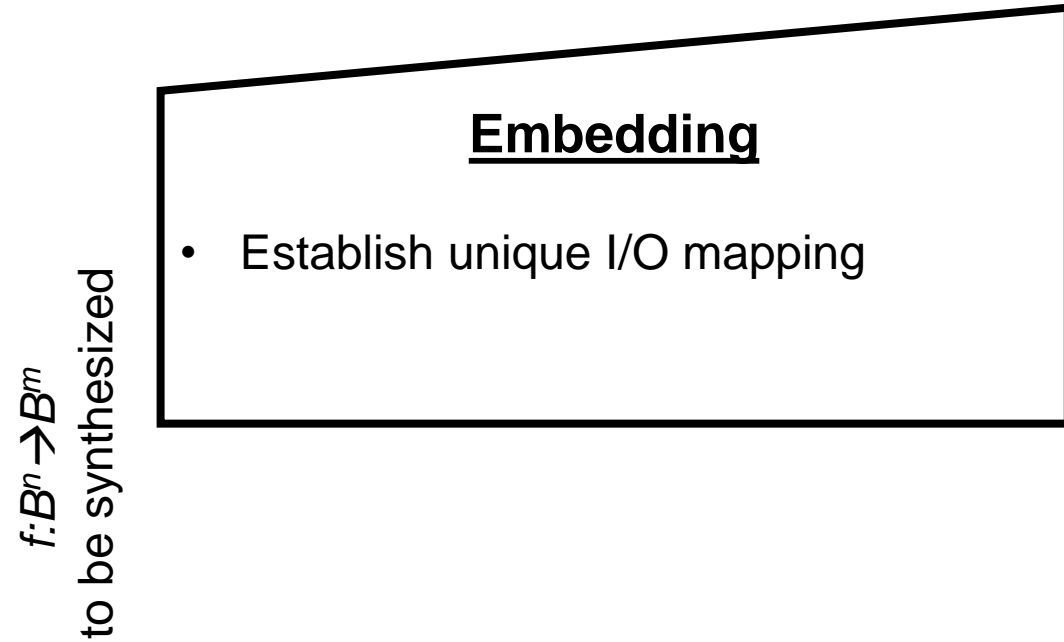

THE EMBEDDING PROBLEM

■ How to describe conventional logic?


| C_{in} | x | y | C_{out} | sum | |
|----------|---|---|-----------|-----|---|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | ? |
| 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | ? |
| 1 | 1 | 1 | 1 | 1 | 1 |

■ Adding $\lceil \log M \rceil$ outputs where M is the largest number of equal output patterns

THE EMBEDDING PROBLEM


| a | c _{in} | x | y | c _{out} | sum | g ₁ | g ₂ |
|---|-----------------|---|---|------------------|-----|----------------|----------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

HOW TO DESIGN REVERSIBLE LOGIC?

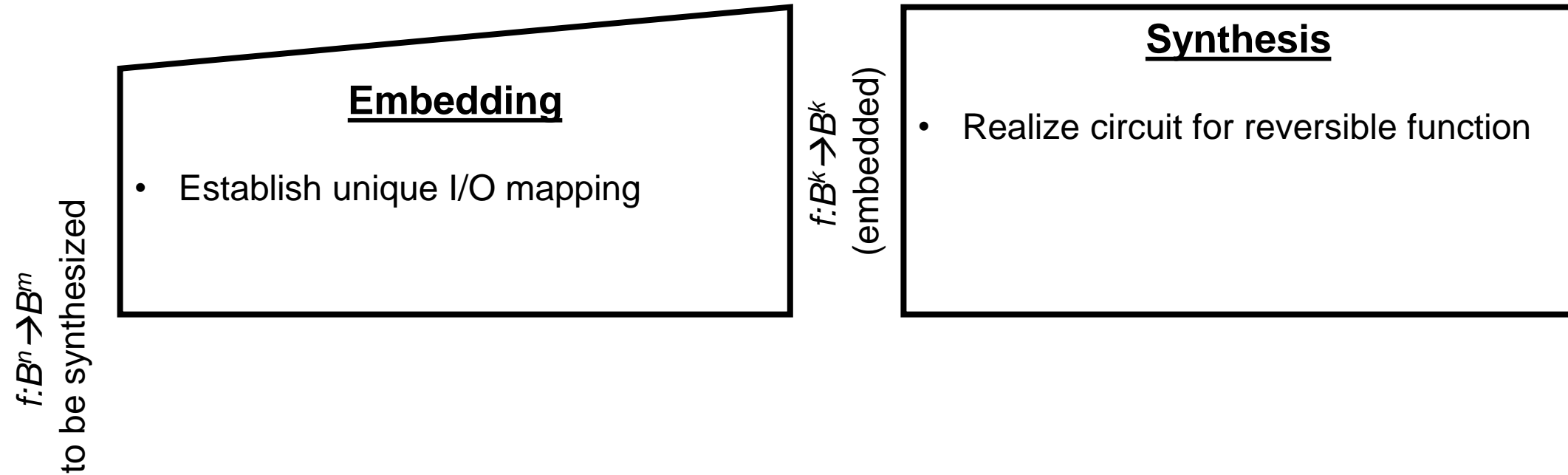


SYNTHESIS

| line (<i>i</i>) | input abcd | output abcd | 1 st step abcd | 2 nd step abcd | 3 rd step abcd |
|----------------------|---------------|----------------|------------------------------|------------------------------|------------------------------|
| 0 | 0000 | 0000 | 0000 | 0000 | 0000 |
| 1 | 0001 | 0111 | 0101 | 0001 | 0001 |
| 2 | 0010 | 0110 | 0110 | 0110 | 0010 |
| 3 | 0011 | 1001 | 1011 | 1111 | 1011 |
| 4 | 0100 | 0100 | 0100 | 0100 | 0100 |
| 5 | 0101 | 1011 | 1001 | 1101 | 1101 |
| 6 | 0110 | 1010 | 1010 | 1010 | 1110 |
| 7 | 0111 | 1101 | 1111 | 1011 | 1111 |
| 8 | 1000 | 1000 | 1000 | 1000 | 1000 |
| 9 | 1001 | 1111 | 1101 | 1001 | 1001 |
| 10 | 1010 | 1110 | 1110 | 1110 | 1010 |
| 11 | 1011 | 0001 | 0011 | 0111 | 0011 |
| 12 | 1100 | 1100 | 1100 | 1100 | 1100 |
| 13 | 1101 | 0011 | 0001 | 0101 | 0101 |
| 14 | 1110 | 0010 | 0010 | 0010 | 0110 |
| 15 | 1111 | 0101 | 0111 | 0011 | 0111 |

 


SYNTHESIS



| line (<i>i</i>) | input abcd | output abcd | 6 th step abcd |
|----------------------|---------------|----------------|------------------------------|
| 0 | 0000 | 0000 | 0000 |
| 1 | 0001 | 0111 | 0001 |
| 2 | 0010 | 0110 | 0010 |
| 3 | 0011 | 1001 | 0011 |
| 4 | 0100 | 0100 | 0100 |
| 5 | 0101 | 1011 | 0101 |
| 6 | 0110 | 1010 | 0 110 |
| 7 | 0111 | 1101 | 0 111 |
| 8 | 1000 | 1000 | 1000 |
| 9 | 1001 | 1111 | 1001 |
| 10 | 1010 | 1110 | 1010 |
| 11 | 1011 | 0001 | 1011 |
| 12 | 1100 | 1100 | 1100 |
| 13 | 1101 | 0011 | 1101 |
| 14 | 1110 | 0010 | 1 110 |
| 15 | 1111 | 0101 | 1 111 |

 


HOW TO DESIGN REVERSIBLE LOGIC?

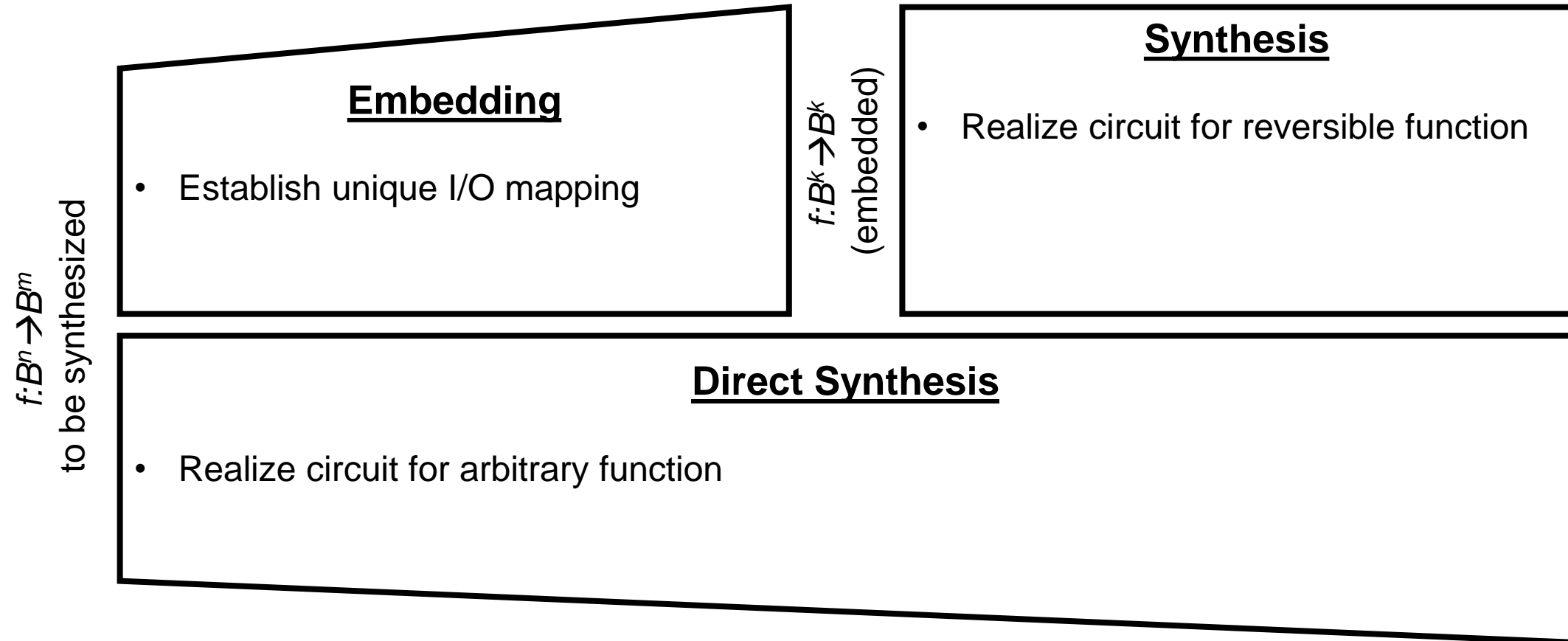

DIRECT SYNTHESIS

  


HOW TO DESIGN REVERSIBLE LOGIC?

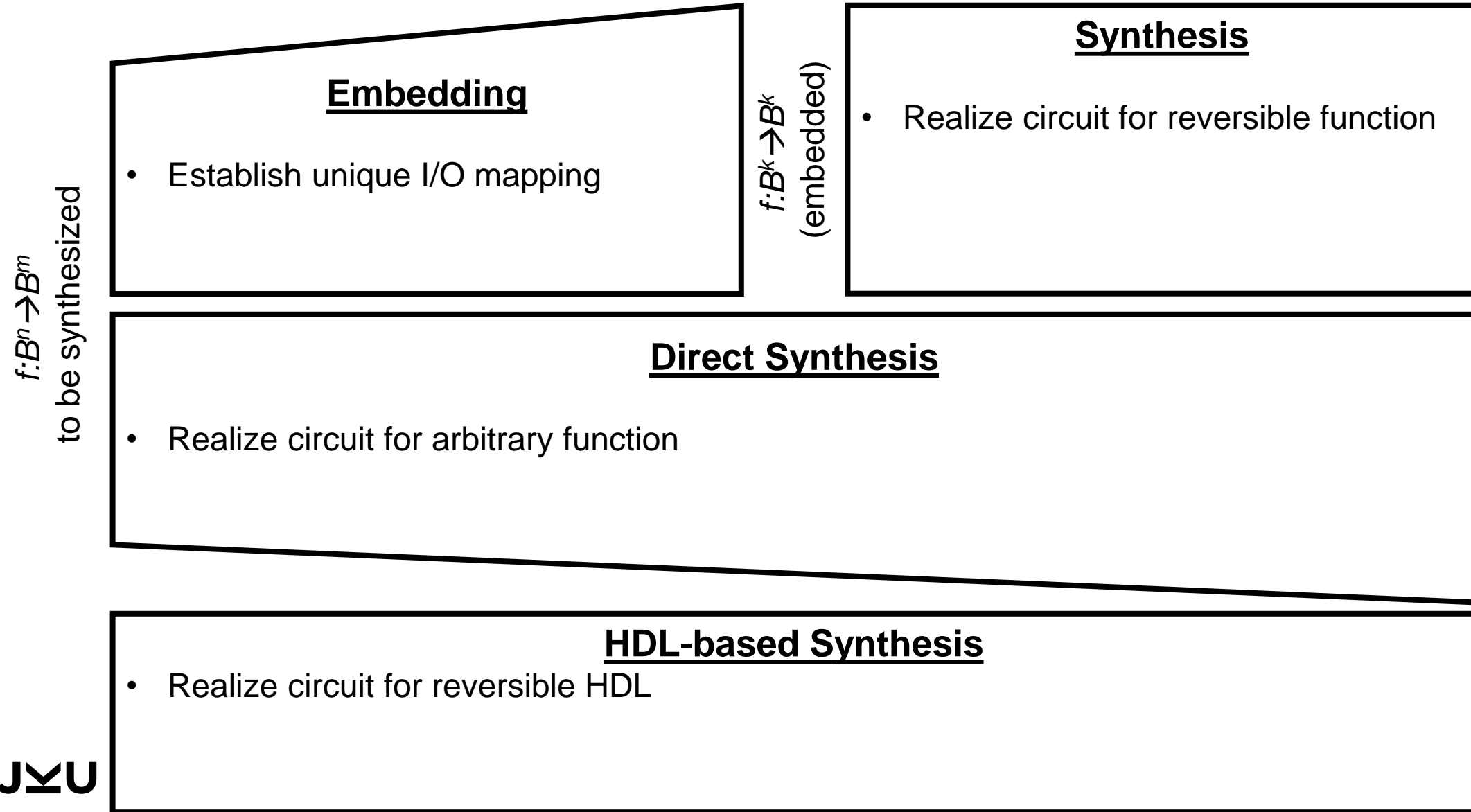


HDL-BASED SYNTHESIS


■ Reversible assignment operations

 

■ Binary operations

 

HDL-BASED SYNTHESIS

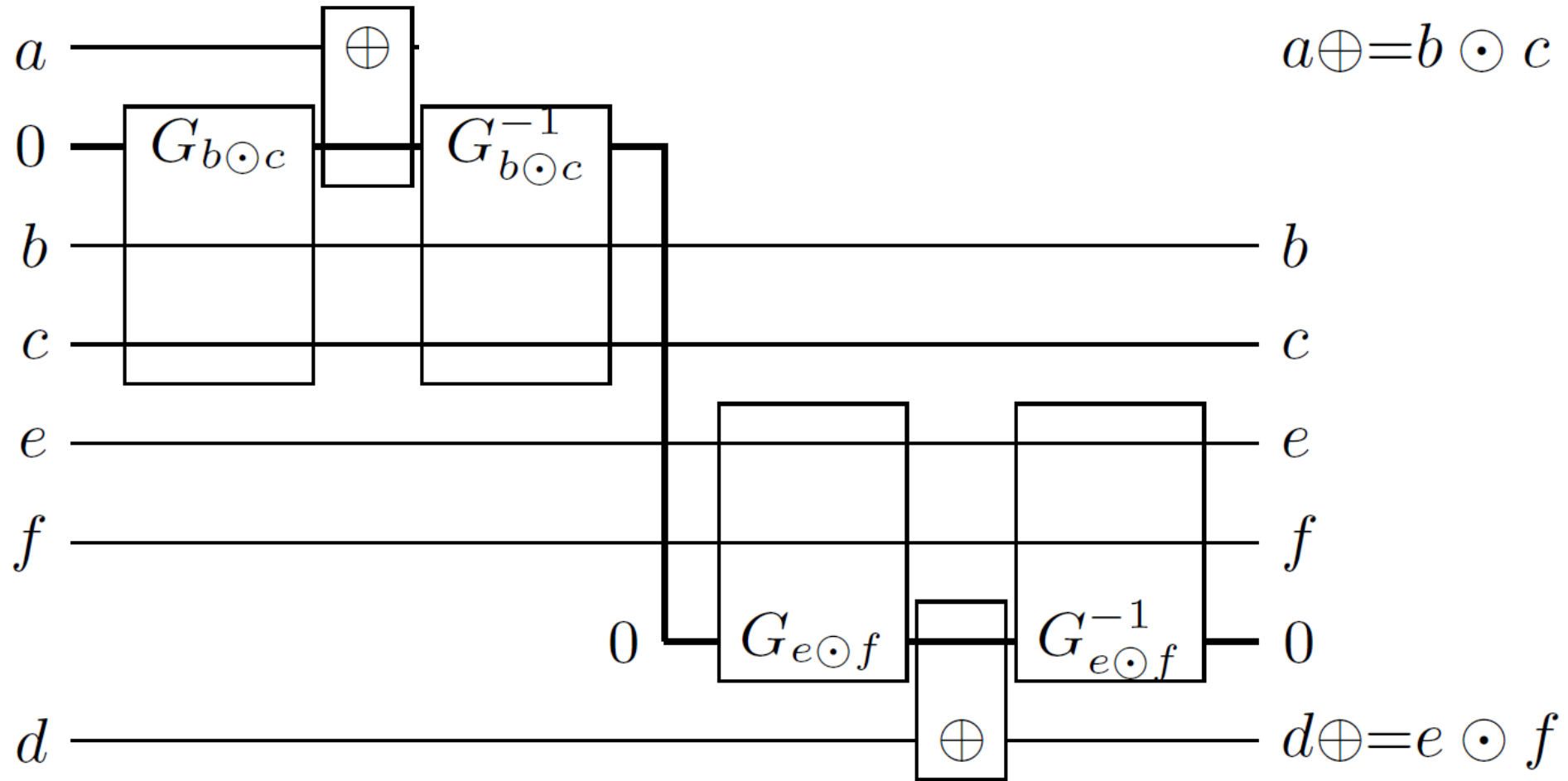

OUTLINE


- What is Reversible Logic?

- ~~■ Why Reversible Logic?~~ → Tomorrow (Applications)

- How to Design of Reversible Logic?

- What's Next?

SUMMARY: DESIGN OF REVERSIBLE CIRCUITS

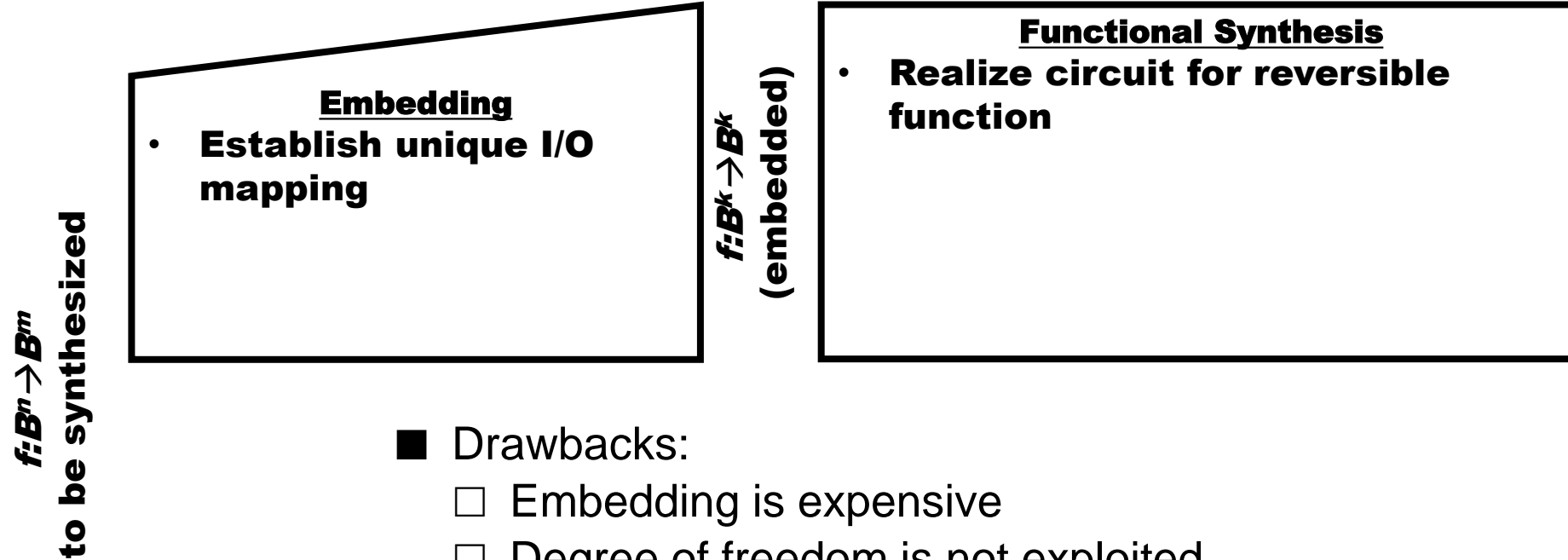


- Drawbacks:
 - ☐ Embedding is expensive
 - ☐ Degree of freedom is not exploited
 - ☐ Exponential growth of representation
- Alternative: One-pass Synthesis

ONE-PASS SYNTHESIS

■ Example: Transformation-based Synthesis

| line (<i>i</i>) | input xy | output xy |
|----------------------|-------------|--------------|
| 0 | 00 | 00 ✓ |
| 1 | 01 | 01 ✓ |
| 2 | 10 | 10 ✓ |
| 3 | 11 | 11 ✓ |

 

■ Start synthesis without embedding

■ Modify function if problem occurs


□ Store changes on buffer line

■ Revert changes after synthesis

□ One gate for each buffer line

■ Can be applied to many different synthesis approaches!


SUMMARY: DESIGN OF REVERSIBLE CIRCUITS

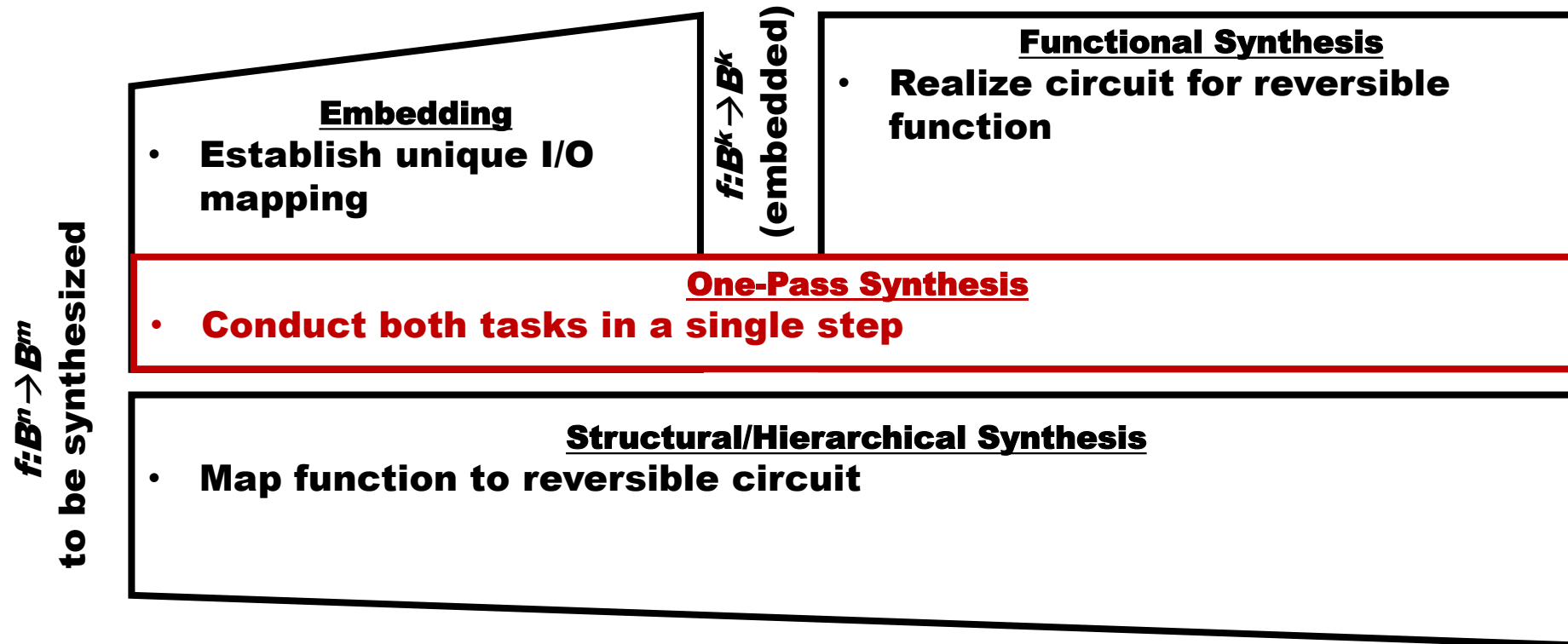

■ Alternative data-structures?

REPRESENTATION OF REVERSIBLE FUNCTIONS

 - Quantum Multiple-valued Decision Diagrams
(publicly available at <http://www.informatik.uni-bremen.de/agra/eng/qmdd.php>)



ADJUSTED DESIGN OF REVERSIBLE CIRCUITS

- Work with permutation matrices!
 - Suitable representation for reversible functionality
 - Can efficiently be represented and manipulated using QMDDs

EXAMPLE: DETERMINATION OF #GARBAGE

- Determine the number of garbage outputs
 - Counting the number of 1's in all rows
 - Equal to multiplying matrix M with transposition of M

| | | Inputs | | | |
|---------|------------------|--------|----|----|----|
| Outputs | $x \backslash y$ | 00 | 01 | 10 | 11 |
| | 00 | 1 | 0 | 0 | 0 |
| | 01 | 0 | 1 | 1 | 0 |
| | 10 | 0 | 0 | 0 | 1 |
| | 11 | 0 | 0 | 0 | 0 |

(a) M

EXAMPLE: DETERMINATION OF #GARBAGE

- Determine the number of garbage outputs
 - Counting the number of 1's in all rows
 - Equal to multiplying matrix M with transposition of M

$$\begin{array}{c} \text{Outputs} \end{array}
 \begin{array}{c} x \quad y \\ \begin{array}{c} \text{ } \\ \text{ } \end{array} \end{array}
 \begin{array}{c} \text{Inputs} \\ \begin{array}{c} 00 \quad 01 \quad 10 \quad 11 \end{array} \end{array}
 \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

(a) M

\times

$$\begin{array}{c} \text{Inputs} \end{array}
 \begin{array}{c} x \quad y \\ \begin{array}{c} \text{ } \\ \text{ } \end{array} \end{array}
 \begin{array}{c} \text{Outputs} \\ \begin{array}{c} 00 \quad 01 \quad 10 \quad 11 \end{array} \end{array}
 \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{bmatrix}$$

(b) M^T


$=$

$$\begin{array}{c} \text{Outputs} \end{array}
 \begin{array}{c} x \quad y \\ \begin{array}{c} \text{ } \\ \text{ } \end{array} \end{array}
 \begin{array}{c} \text{Inputs} \\ \begin{array}{c} 00 \quad 01 \quad 10 \quad 11 \end{array} \end{array}
 \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 2 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

 
(c) $D = M \cdot M^T$

QMDDS: FURTHER APPLICATIONS

- Embedding
- Synthesis
- Verification
- Simulation
- ...




SUMMARY: DESIGN OF REVERSIBLE CIRCUITS

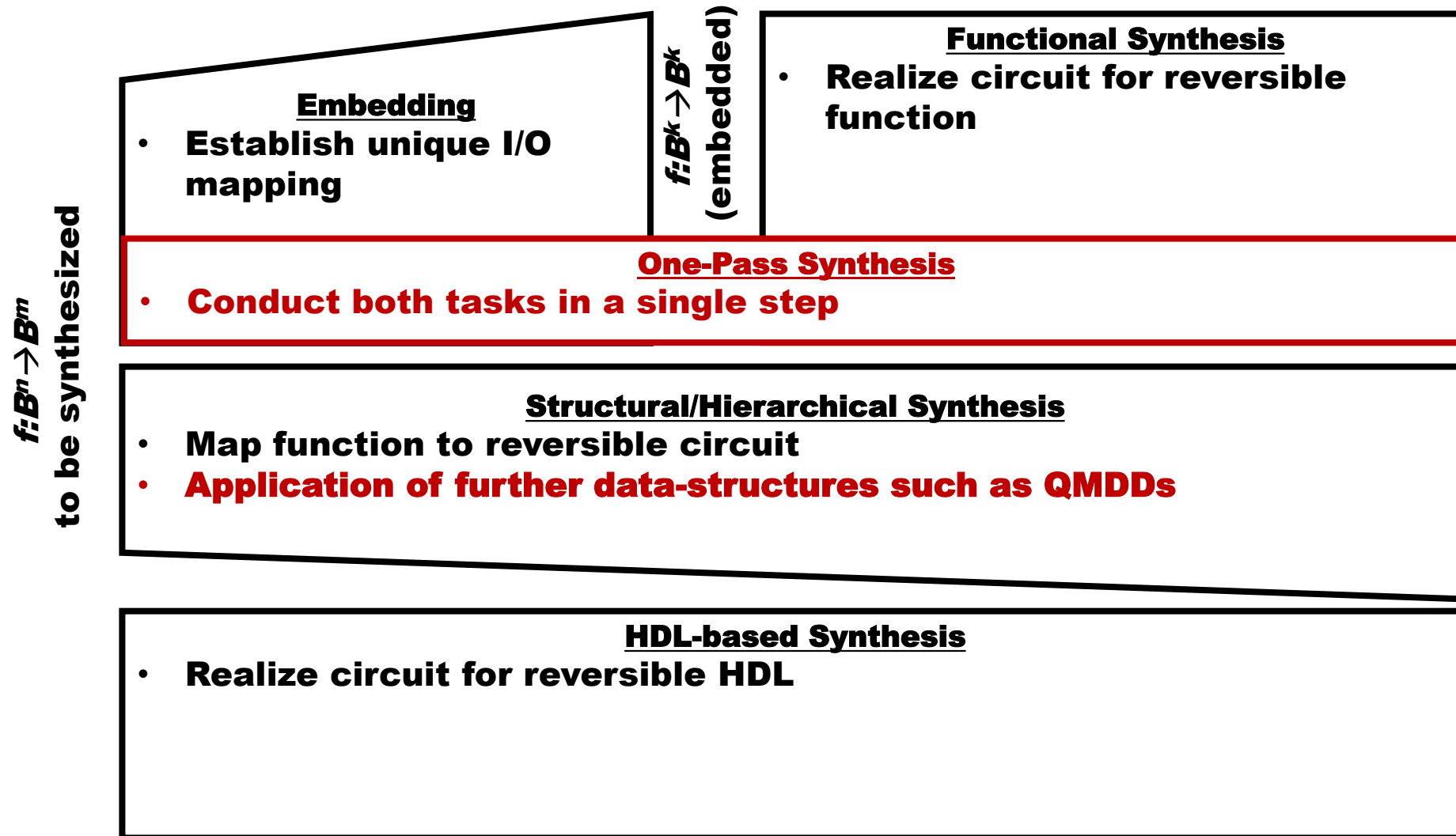

HDL-BASED SYNTHESIS

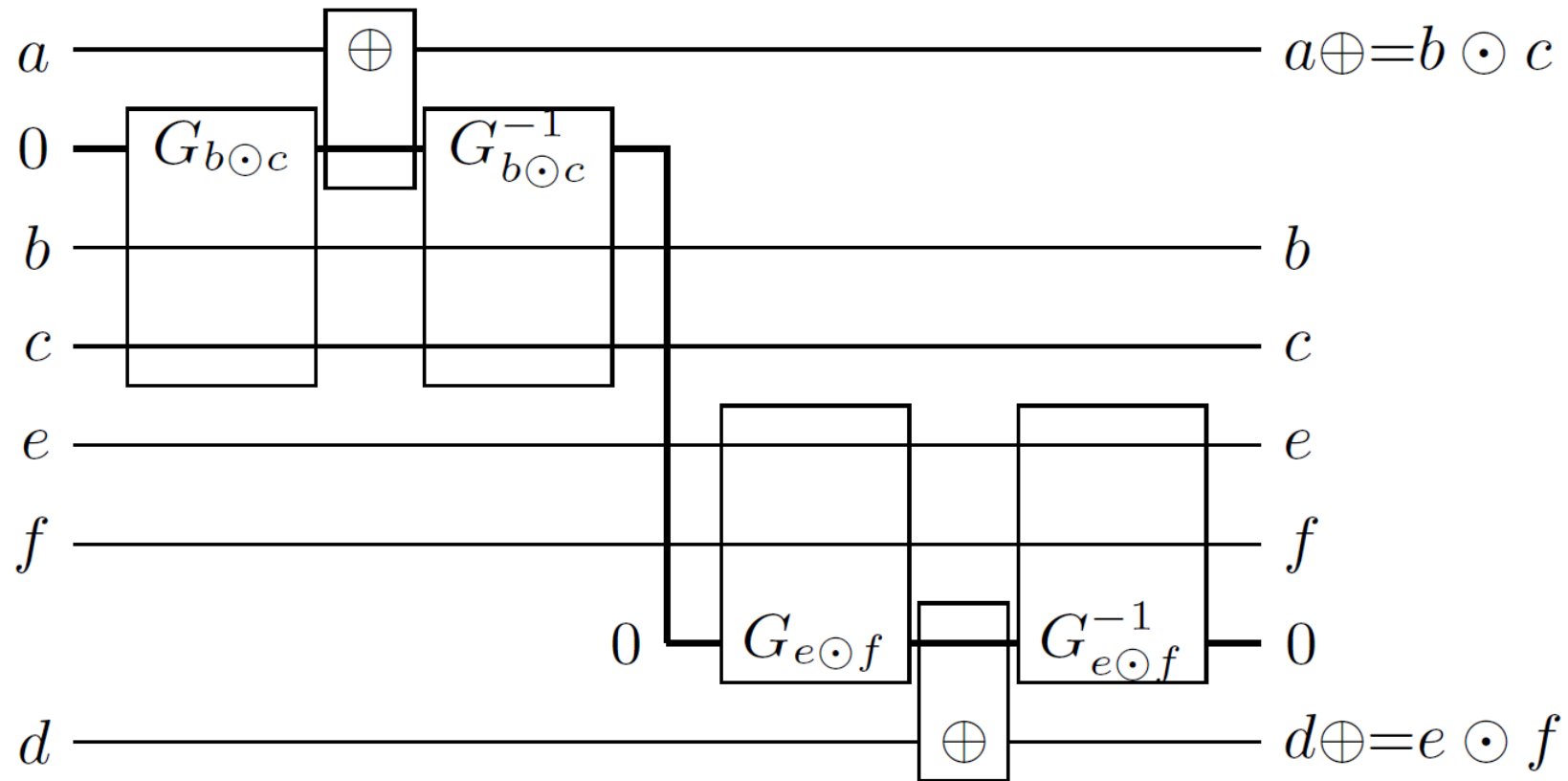- Distinction between reversible assignment operations and binary operations




GENERAL OBSERVATIONS

- Reversible HDL descriptions are inherently reversible
- ➔ There must be a reversible circuit with zero additional lines realizing the described functionality

SEQUENCE OF STATEMENTS

 - Consider a sequence of three statements
- Assume their realization requires 1, 6, and 4 additional lines



➔ Focus on optimizing the realization of the “largest” statement!

SIMPLE OPTIMIZATION

$$a += ((b \& c) + ((d * e) - f))$$

- Intermediate results of the inner expressions must be buffered
- Considering 32-bit signals, this requires 96 circuit lines
- Plus 32 circuit lines to buffer the result of the outer expression
- → 128 circuit lines in total



$$\begin{aligned} a &+= (b \& c); \\ a &+= (d * e); \\ a &-= f; \end{aligned}$$

- Binary operations are applied separately with an assignment operation.
- Hence, no more than 32 circuit lines are needed to buffer the intermediate results

GENERAL OBSERVATIONS

- Reversible HDL descriptions are inherently reversible
- ➔ There must be a reversible circuit with zero additional lines realizing the described functionality
- Thus far: The realization of the assignment and the expression is considered separately

$$\hat{c} = a \& b$$

  

- ➔ Not possible for each combination of assignment/expr.

REVERSIBLE HDL-BASED SYNTHESIS

- **Scalable** synthesis of **efficient** circuits
is THE big challenge in reversible circuit design
- Does not necessarily require a fully-fledged HDL-synthesizer
- Not so much about generating building blocks, but using/combining them in a clever fashion
- Use of techniques from compiling, term re-writing, etc.

SUMMARY: DESIGN OF REVERSIBLE CIRCUITS

