 


APPLICATION OF SYNTHESIS APPROACHES



Robert Wille

Johannes Kepler University Linz, Austria

robert.wille@jku.at

FURTHER READING

■ **Adiabatic Circuits**

Foundations of Generalized Reversible Computing, RC 2017

Exploiting Reversible Logic Design for Implementing Adiabatic Circuits, MIXDES 2017

■ **Encoder Design**

Taking One-to-one Mappings for Granted: Advanced Logic Design of Encoder Circuits, DATE 2017

Synthesis of Approximate Coders for On-chip Interconnects Using Reversible Logic, DATE 2016

Automatic Design of Low-Power Encoders Using Reversible Circuit Synthesis, DATE 2012

■ **Simulation**

Exploiting Reversibility in the Complete Simulation of Reversible Circuits, AFRICON 2013

■ **ATPG**

A Family of Logical Fault Models for Reversible Circuits, ATS 2015

■ **Verification**

Exploiting Inherent Characteristics of Reversible Circuits for Faster Combinational Equivalence Checking, DATE 2016

APPLICATIONS

- Quantum Computation

APPLICATIONS

■ ~~Quantum Computation~~ → Later today

APPLICATIONS

- ~~Quantum Computation~~ → Later today
- Low Power Design

LOW POWER DESIGN #1

■ Rolf Landauer (1961):

Deletion of a single bit leads to a power dissipation of $W = kT \ln 2$

T ...Temperature

k ...Boltzmann-Constant

$(1,381 \cdot 10^{-23} \text{ J/K})$


■ Charles H. Bennett (1973):

Circuits without energy dissipation have to be reversible

LOW POWER DESIGN #2

Important:

 Does not mean that each implementation of a reversible circuit is “automatically” power-efficient!
→ How to exploit reversibility for reducing power dissipation still open research problem



Landauer's Barrier



Less power consumption is only possible if computation is reversible

APPLICATIONS

- ~~Quantum Computation~~ → Later today
- Low Power Design
- Adiabatic Circuits

ADIABATIC CIRCUITS

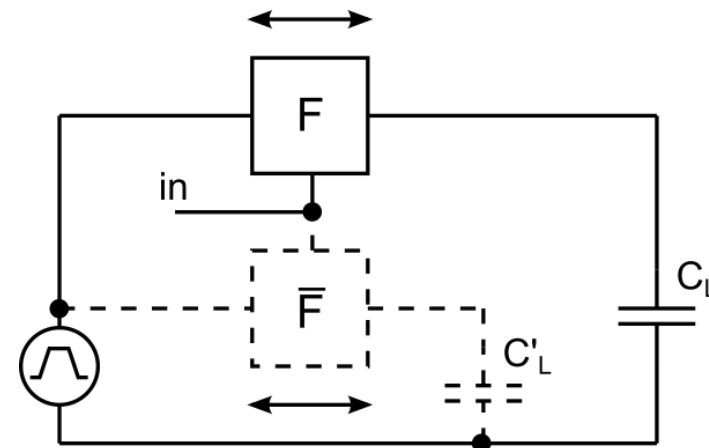 - adiabatic (from Thermodynamics)
 - no transfer of heat or matter into or out of the system
- adiabatic (in electronics)
 - no (or minimal) energy loss



ADIABATIC CHARGING

$$V_C(t) = \frac{1}{C} \int I(t) dt = \frac{1}{C} I_{avg}(t) t$$

$$I_{avg}(t) = \frac{C V_C(t)}{t}$$

$$E_{diss} = R \int_0^T I(t)^2 dt \geq R \int_0^T I_{avg}(t)^2 dt = R I_{avg}(T)^2 T = \frac{RC}{T} C V_C(T)^2$$

■ Supply Voltage


- ☐ ramping up the voltage results in a constant current

■ additional Rules

- ☐ Never turn on a transistor if there is a voltage difference between drain and source.
- ☐ Never turn off a transistor if there is a current through it.


COMPLEX ADIABATIC CIRCUITS

■ pipeline structure

 



■ To respect the rules mentioned

 - ☐ A must not change until B has been charged and discharged
- ☐ B must not change until C has been charged and discharged





SEPARATE DISCHARGE PATH

  - Input is allowed to change before discharge phase
- Signal has no longer to propagate through whole chain and back





DISCHARGE PATH

  - Never turn on a transistor if there is a voltage difference between drain and source
- Discharge ONLY when charged!
 - State (charged/uncharged) of cell F can be determined by output of following cell G via function G^{-1}
 - Output of following cell G controls discharge path of F
 - G must be reversible to realize G^{-1}



DISCHARGE PATH

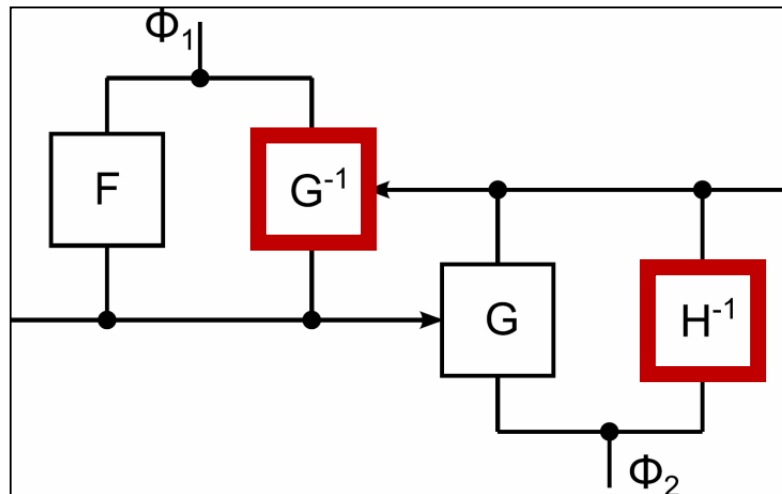 - Never turn on a transistor if there is a voltage difference between drain and source
- Discharge ONLY when charged!
 - State (charged/uncharged) of cell F can be determined by output of following cell G via function G^{-1}
 - Output of following cell G controls discharge path of F
 - **G must be reversible to realize G^{-1}**



APPLICATIONS

- ~~Quantum Computation~~ → Later today
- Low Power Design
- Adiabatic Circuits
- Encoders

ENCODERS

■ Complete

$x_3x_2x_1$	$x_3x_2x_1$
000	000
001	101
010	011
011	111
100	010
101	100
110	110
111	001

■ Incomplete

$x_3x_2x_1$	$x_3x_2x_1$
000	000
001	—
010	010
011	—
100	—
101	001
110	—
111	—

■ Application-specific

$x_3x_2x_1$	Hw	$x_3x_2x_1$
000	1	001
001	0	000
010	2	011
011	3	111
100	2 \Rightarrow	110
101	1	010
110	2	101
111	1	100

■ Challenges


- ☐ Exponential Complexity
- ☐ Guaranteeing one-to-one mappings
- ☐ Exploiting the full degree of freedom



$$\sum_{i=0}^m \binom{m}{i}$$

USING REVERSIBLE LOGIC

 ■ Reversible circuits: Get a 1:1 mapping “for free”!




■ Challenges


- ☐ Exponential Complexity
- ☒ Guaranteeing one-to-one mappings
- ☐ Exploiting the full degree of freedom

USING REVERSIBLE LOGIC

■ State-of-the-art:

 

■ Using Reversible Logic:

 

■ Application-specific

$x_3x_2x_1$	Hw	$x_3x_2x_1$
000	1	001
001	0	000
010	2	011
011	3	111
100	2	110
101	1	010
110	2	101
111	1	100


\Rightarrow

■ Challenges

- ☐ Exponential Complexity
- ☒ Guaranteeing one-to-one mappings
- ☒ Exploiting the full degree of freedom

USING REVERSIBLE LOGIC

■ QMDDs

 

		Inputs							
		x_1	x_2	x_3					
		000	001	010	011	100	101	110	111
Outputs	000	0	0	0	1	0	0	0	0
	001	0	0	0	0	0	0	1	0
	010	0	1	0	0	0	0	0	0
	011	0	0	0	0	1	0	0	0
	100	0	0	0	0	0	1	0	0
	101	0	0	1	0	0	0	0	0
	110	0	0	0	0	0	0	0	1
	111	1	0	0	0	0	0	0	0


■ Challenges

- ✓ Exponential Complexity
- ✓ Guaranteeing one-to-one mappings
- ✓ Exploiting the full degree of freedom

APPLICATIONS

- ~~Quantum Computation~~ → Later today
- Low Power Design
- Adiabatic Circuits
- Encoders
- Further
 - Complete Simulation

COMPLETE SIMULATION

 


→ Run-time complexity: $2^n d$
 (n: number of line; d: number of gates)

EXPLOITING REVERSIBILITY

- Functional effect of single gates
- For many input pattern, single gates have no effect (only patterns with control lines set to 1)
- Reversible gates realize permutations
- If an input pattern 0000 maps to the output 0001, then 0001 also maps to 0000
 - Each gate eventually leads to an exchange of patterns

EXPLOITING REVERSIBILITY

 


Input patterns with effect:

$g_1: 2$	$g_4: 8$
$g_2: 16$	$g_5: 16$
$g_3: 8$	$g_6: 4$

- Reversible gates realize permutations
 - g_1 : Swaps 1110 and 1111
 - ...
 - g_6 : Swaps all pattern of the form 11-1 with corresponding pattern of the form 10-1

EXPLOITING REVERSIBILITY

 

Input patterns with effect:

$g_1: 2$


- Reversible gates realize permutations
 - g_1 : Swaps 1110 and 1111
- ➔ Simulation of g_1 requires a single swap operation (compared to 16 simulation steps)

APPLICATIONS

- ~~Quantum Computation~~ → Later today
- Low Power Design
- Adiabatic Circuits
- Encoders
- Further
 - Complete Simulation
 - ATPG



TEST OF REVERSIBLE CIRCUITS

 - Generate an input assignment that
 - ☐ triggers the faulty behavior (controlability)
 - ☐ shows the faulty behavior (observability)



- In general easy for reversible circuits
(except additional restrictions like constant inputs need to be considered)

DESIGN FOR TESTABILITY

  

APPLICATIONS

- ~~Quantum Computation~~ → Later today
- Low Power Design
- Adiabatic Circuits
- Encoders
- Further
 - ☐ Complete Simulation
 - ☐ ATPG
 - ☐ Verification

VERIFICATION/ EQUIVALENCE CHECKING

- Full connectivity
(verification by simulation is more promising)

Circuit	No. lines	No. gates	Runtime (conv.)	Runtime (rand. sim.)	No. pattern
alu	101	4472	>500.00	0.03	7
avg16	274	1601	>500.00	0.01	4
avg16	546	3297	>500.00	0.04	3
avg8	147	860	>500.00	0.00	2
avg16	138	753	44.54	0.00	5
apex5	240	3307	42.10	0.06	7
cps	31	2668	26.40	0.03	9
ex1010	196	2981	23.93	0.03	2
table3	109	1987	16.66	0.08	572
pdc	178	2079	14.88	0.03	83
avg8	291	1772	12.97	0.01	2

VERIFICATION/ EQUIVALENCE CHECKING

- Full connectivity
(verification by simulation is more promising)
- Search space is smaller
- Reversible Miter (ff^{-1})

VERIFICATION/ EQUIVALENCE CHECKING

- Full connectivity
(verification by simulation is more promising)
- Search space is smaller
- Reversible Miter (ff^{-1})
- XOR-richness
- Undo computations when an error occurred
- ...

APPLICATIONS

- ~~Quantum Computation~~ → Later today
- Low Power Design
- Adiabatic Circuits
- Encoders
- Further
 - ☐ Complete Simulation
 - ☐ ATPG
 - ☐ Verification